

2


Mathematical Modeling of Mechanical & Electrical System

classmate
Date _____
Page _____

* Mathematical Modeling of Mechanical System

Example 3.1


@ Parallel

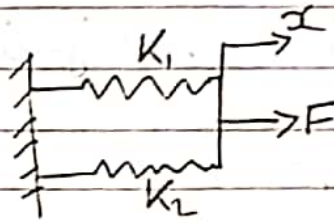

$$F = K_{eq} x = K_1 x + K_2 x$$

$$\Rightarrow \boxed{K_{eq} = K_1 + K_2}$$

⑥ Series

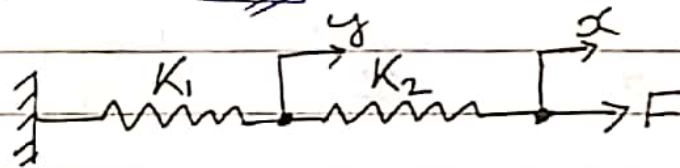

$$F = K_{eq} x$$

$$F = K_1 y = K_2 (x - y)$$

$$\Rightarrow K_1 y = K_2 x - K_2 y$$


$$y = \frac{K_2 x}{K_1 + K_2}$$

$$\boxed{\frac{1}{K_{eq}} = \frac{1}{K_1} + \frac{1}{K_2}}$$

$$\frac{K_1 K_2 x}{K_1 + K_2} = K_{eq} x \Rightarrow K_{eq} = \frac{K_1 K_2}{K_1 + K_2}$$

Example 3.2

(a)

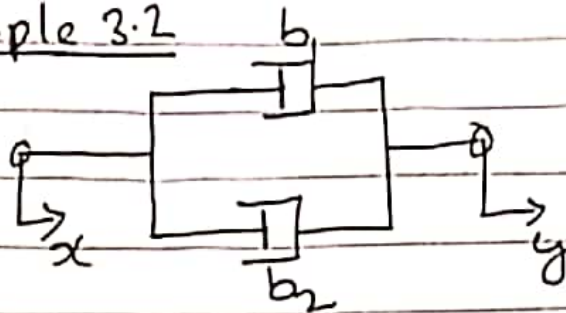


$$f = b_1(\dot{y} - \dot{x}) + b_2(\dot{y} - \dot{x}) = (b_1 + b_2)(\dot{y} - \dot{x})$$

$$f = b_{eq}(\dot{y} - \dot{x})$$

$$\text{So } \boxed{b_{eq} = b_1 + b_2}$$

(c)

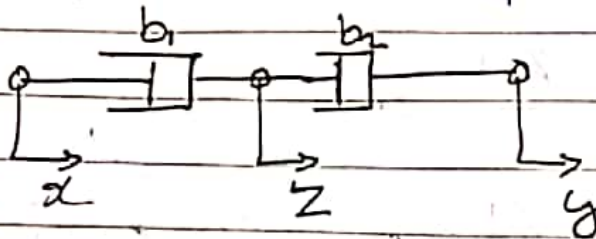

$$f = b_{eq}(\dot{y} - \dot{x})$$

$$f = b_1(\dot{z} - \dot{x}) = b_2(\dot{y} - \dot{z})$$

$$b_1\dot{z} - b_1\dot{x} = b_2\dot{y} - b_2\dot{z}$$

$$(b_1 + b_2)\dot{z} = b_2\dot{y} + b_1\dot{x} - (b_1 + b_2)\dot{x}$$

$$(b_1 + b_2)(\dot{z} - \dot{x}) = b_2\dot{y} - b_2\dot{x}$$

$$(\dot{z} - \dot{x}) = \frac{b_2}{b_1 + b_2}(\dot{y} - \dot{x})$$

$$\frac{b_1 b_2}{b_1 + b_2} (\dot{y} - \dot{x}) = b_{eq} (\dot{y} - \dot{x})$$

$$b_{eq} = \frac{b_1 b_2}{b_1 + b_2} \Rightarrow \boxed{\frac{1}{b_{eq}} = \frac{1}{b_1} + \frac{1}{b_2}}$$


Dashpot: A dashpot is a mechanical device, a damper which resists motion via viscous friction.

↳ The resulting force is proportional to the velocity, but acts in the opposite direction, slowing the motion and absorbing energy.

$$\text{---} \square \rightarrow F = bV/b\dot{x}$$

Example 3.3:

PTO

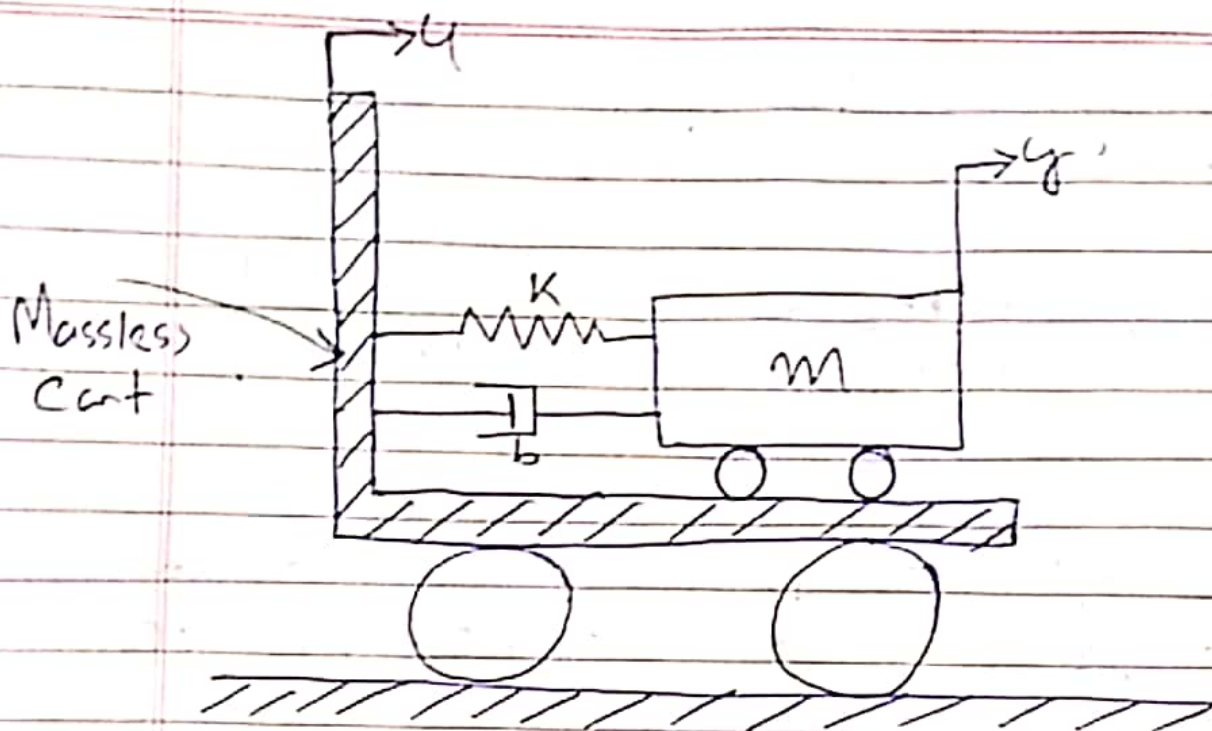

\Rightarrow Cart is standing still at $t < 0$

\Rightarrow Spring-mass-dashpot system on the cart is also standing still $\forall t < 0$

$u(t)$: Input {displacement of cart}

at $t=0$ $\dot{u} = \text{Constant}$

$y(t)$: Output {displacement of mass relative to ground}


$$-K(y-u) - b\left(\frac{dy}{dt} - \frac{du}{dt}\right) = m \frac{d^2y}{dt^2}$$

$$\Rightarrow m \frac{d^2y}{dt^2} + b \frac{dy}{dt} + Ky = b \frac{du}{dt} + Ku$$

$$(ms^2 + bs + K)Y(s) = (bs + K)U(s)$$

$$G(s) = \frac{Y(s)}{U(s)} = \frac{bs + K}{ms^2 + bs + K}$$

Example 3.4:

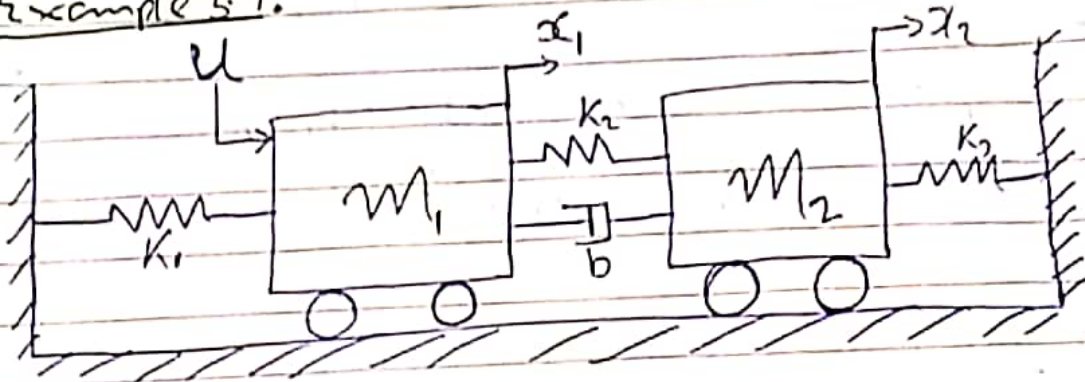

U is the external force applied and x_1 & x_2 represents position of m_1 & m_2 respectively.

Input: U

Output: x_1 & x_2

$$U - K_1 x_1 - K_2 (x_1 - x_2) - b(\dot{x}_1 - \dot{x}_2) = m_1 \ddot{x}_1 \quad \text{--- ①}$$

$$-K_3 x_2 - K_2 (x_2 - x_1) - b(\dot{x}_2 - \dot{x}_1) = m_2 \ddot{x}_2 \quad \text{--- ②}$$

Equation ① & ② is the mathematical model of the given system.


$$U(s) - K_1 X_1(s) - K_2 (X_1(s) - X_2(s)) - bs(X_1(s) - X_2(s)) \\ = m_1 s^2 X_1(s) \quad \text{--- (1)}$$

$$-K_3 X_2(s) - K_2 (X_2(s) - X_1(s)) - bs(X_2(s) - X_1(s)) \\ = m_2 s^2 X_2(s) \quad \text{--- (2)}$$

$$\frac{X_1(s)}{U(s)} = \frac{m_2 s^2 + bs + K_2 + K_3}{(m_1 s^2 + bs + K_1 + K_2)(m_2 s^2 + bs + K_2 + K_3) - (bs + K_2)^2}$$

$$\frac{X_2(s)}{U(s)} = \frac{bs + K_2}{(m_1 s^2 + bs + K_1 + K_2)(m_2 s^2 + bs + K_2 + K_3) - (bs + K_2)^2}$$

Example 3.5:

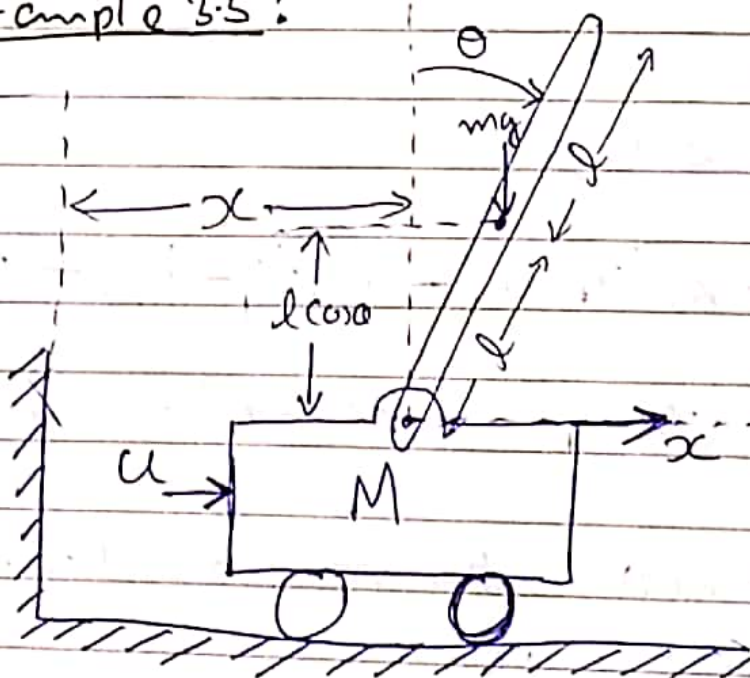

Inverted pendulum: Pendulum that has its Center of mass above its pivot point.


eg \rightarrow human beings

\Rightarrow 2 DOF System (θ, x)

Input force = U

$$x_a = x + l \sin \theta$$

$$y_a = l \cos \theta$$

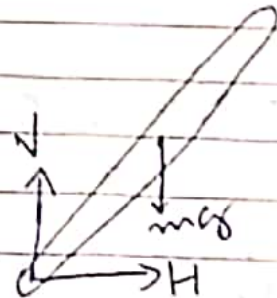

$$I \ddot{\theta} = V l \sin \theta - H l \cos \theta \quad \text{--- (1)}$$

$$H = m \frac{d^2}{dt^2} (x + l \sin \theta) \quad \text{--- (2)}$$

$$V - mg = m \frac{d^2}{dt^2} (l \cos \theta) \quad \text{--- (3)}$$

$$M \frac{d^2 x}{dt^2} = U - H \quad \text{--- (4)}$$

The above four equations are the mathematical model of the given system.

⇒ Since the inverted pendulum is kept vertical.
 ↳ θ can be assumed to be close to zero.

$$\begin{aligned} \sin \theta &\approx 0 \\ \cos \theta &\approx 1 \end{aligned} \quad \left\{ \text{linearization} \right\}$$

$$\begin{aligned} I \ddot{\theta} &= V l \theta - H l & \text{--- (1)} \\ m(\ddot{x} + l \ddot{\theta}) &= H & \text{--- (2)} \\ V &= m g & \text{--- (3)} \\ M \ddot{x} &= U - H & \text{--- (4)} \end{aligned} \quad \left\{ \text{linearized Mathematical Model} \right\}$$

⇓ Eliminating H & V

$$(M+m) \ddot{x} + m l \ddot{\theta} = U. \quad \text{--- (a)}$$

$$(I + m l^2) \ddot{\theta} + m l \ddot{x} = m g l \theta \quad \text{--- (b)}$$


$$\left. \begin{aligned} (M+m) s^2 X(s) + m l s^2 \theta(s) &= U(s) \\ (I + m l^2) s^2 \theta(s) + m l s^2 X(s) &= m g l \theta(s) \end{aligned} \right\}$$

★ Mathematical Modeling of Electrical System

Basic laws governing electrical circuit are
Kirchhoff's Law:

- Current Law: Algebraic sum of all currents entering and leaving a node is zero.
- Voltage Law: At any given instant the algebraic sum of the voltage around any loop in an electric circuit is zero.


LRC Circuit

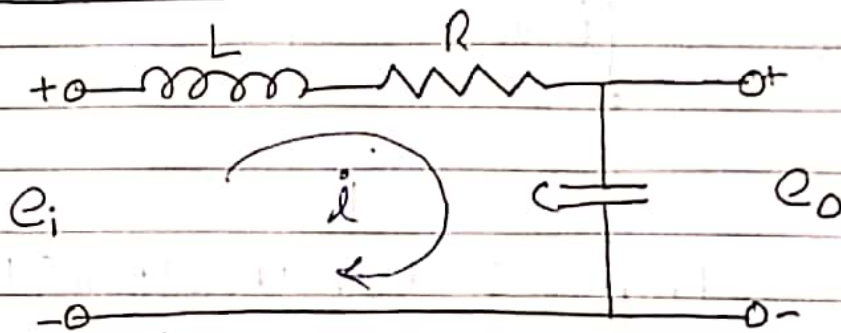

$$-e_i + L \frac{di}{dt} + iR + \frac{1}{C} \int_0^t i dt = 0 \quad \text{--- (a)}$$

$$e_o = \frac{1}{C} \int_0^t i dt \quad \text{--- (b)}$$

$$\boxed{\frac{E_o(s)}{E_i(s)} = \frac{1}{LCs^2 + RCs + 1}}$$

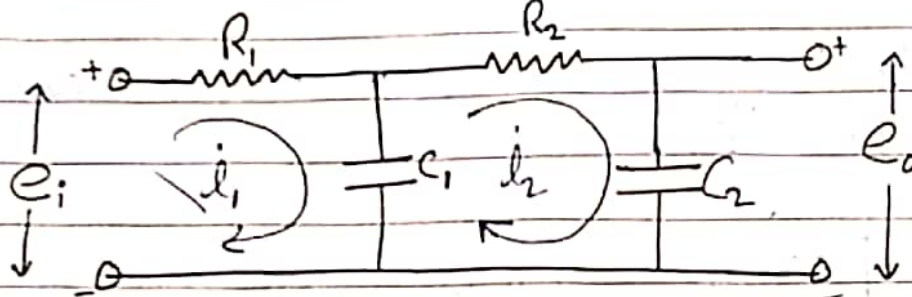
Transfer Function of Cascaded Element

$$-e_i + i_1 R_1 + \frac{1}{C_1} \int_0^t (i_1 - i_2) dt = 0 \quad \text{--- (1)}$$

$$+ \frac{1}{C_1} \int_0^t (i_2 - i_1) dt + i_2 R_2 + \frac{1}{C_2} \int_0^t i_2 dt = 0 \quad \text{--- (2)}$$

$$e_o = \frac{1}{C_2} \int_0^t i_2 dt \quad \text{--- (3)}$$

$$\boxed{\frac{E_o(s)}{E_i(s)} = \frac{1}{R_1 C_1 R_2 C_2 s^2 + (R_1 C_1 + R_2 C_2 + R_1 C_2) s + 1}}$$

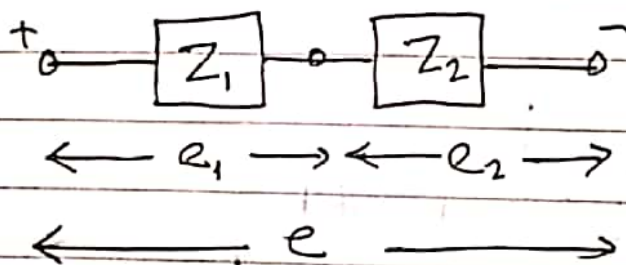Complex Impedance


⇒ For electrical circuit, it is convenient to write the Laplace-transformed equation directly without writing the differential equations.

⇒ The Complex impedance $Z(s)$ of a two-terminal circuit is the ratio of $E(s)$, the Laplace transform of the voltage across the terminals to $I(s)$, the Laplace transform of current through the element.

(Under the assumption initial condition is zero)



<u>Element</u>	<u>Impedance</u>
1) Resistance (R)	R
2) Capacitance (C) $V(t) = \frac{1}{C} \int_0^t i dt$	$\frac{1}{Cs}$
3) Inductance (L) $V(t) = L \frac{di}{dt}$	LS

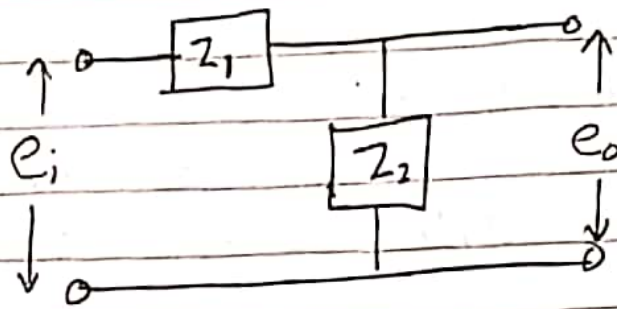⇒ If Complex impedances are connected in series, the total impedance is the sum of the individual complex impedances.



$$\frac{E_o(s)}{E_i(s)} = \frac{Z_2}{Z_1 + Z_2}$$

Example 3.7

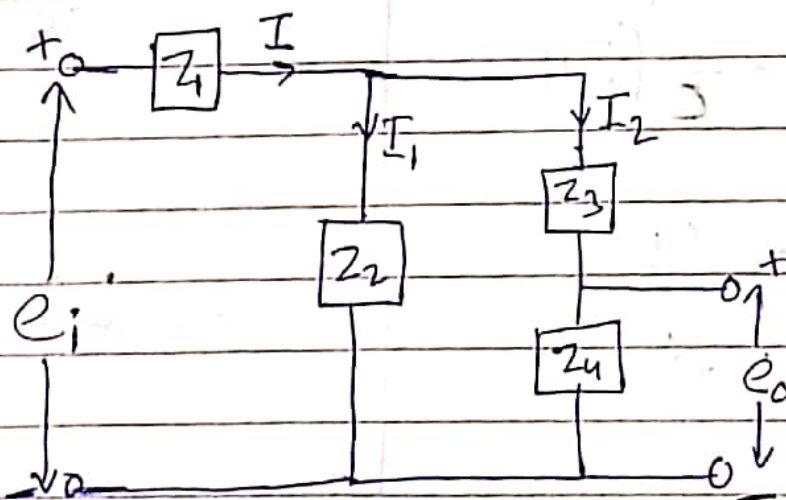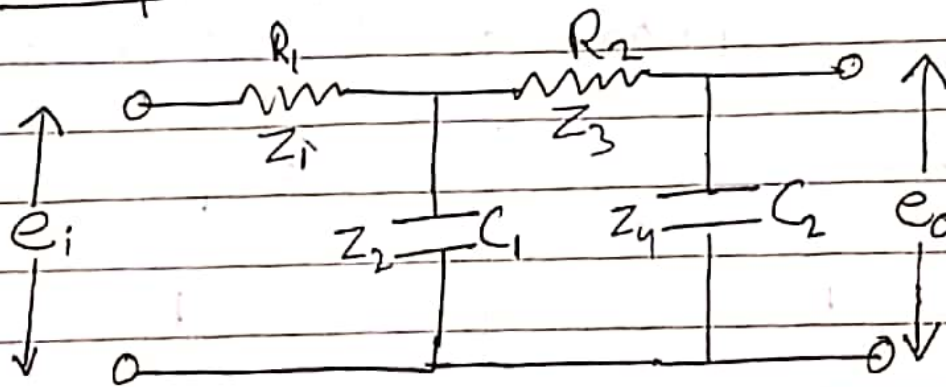

$$I_1 = \frac{Z_3 + Z_4}{Z_2 + Z_3 + Z_4} I$$

$$I_2 = \frac{Z_2}{Z_2 + Z_3 + Z_4} I$$

$$E_i = Z_1 I + Z_2 I_1$$

$$= Z_1 I + \frac{Z_2 (Z_3 + Z_4)}{Z_2 + Z_3 + Z_4} I$$



$$E_o = Z_4 I_2 = \frac{Z_4 Z_2}{Z_2 + Z_3 + Z_4} I$$

$$\frac{E_o}{E_i} = \frac{\frac{Z_4 Z_2}{Z_2 + Z_3 + Z_4}}{Z_1 + \frac{Z_2 (Z_3 + Z_4)}{Z_2 + Z_3 + Z_4}} = \frac{Z_4 Z_2}{Z_1 Z_2 + Z_1 Z_3 + Z_1 Z_4 + Z_2 Z_3 + Z_2 Z_4}$$

$$\frac{E_o(s)}{E_i(s)} = \frac{1}{R_1 C_1 R_2 C_2 s^2 + (R_1 C_1 + R_2 C_2 + R_1 C_2) s + 1}$$

Transfer Function of Nonloading Cascaded Element

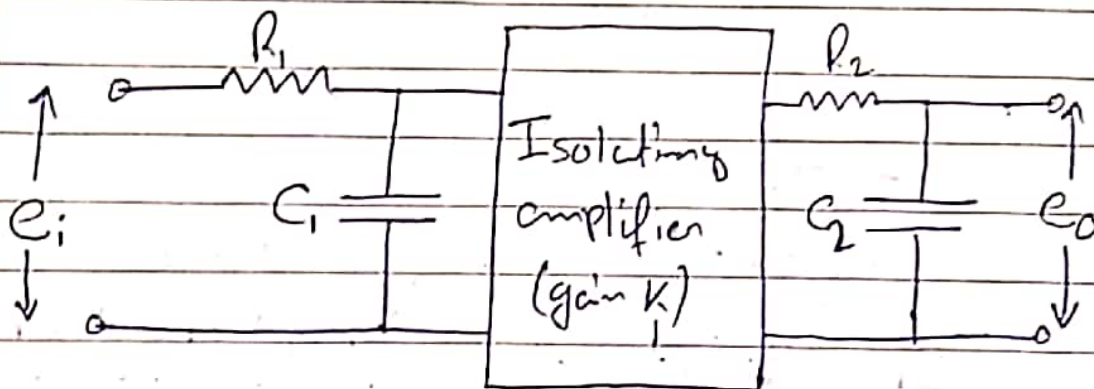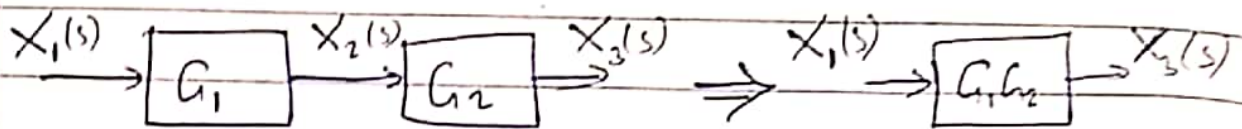⇒ The transfer function of a system consisting of two nonloading cascaded element can be obtained by eliminating the intermediate input & output



$$\frac{E_o(s)}{E_i(s)} = \left(\frac{1}{1 + R_1 C_1 s} \right) K \left(\frac{1}{1 + R_2 C_2 s} \right)$$

$$\frac{E_o(s)}{E_i(s)} = \frac{K}{(1 + R_1 C_1 s)(1 + R_2 C_2 s)}$$


→ Opamp has gain of about $10^5 \sim 10^6$ Vdc/kac

classmate
Date _____
Page _____

Electronic Controllers

Sig-J
(P/L/K/H)

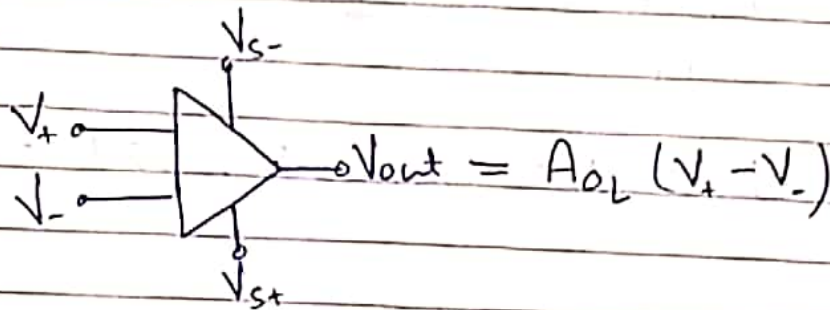
* Operational Amplifiers: It is DC-coupled high-gain electronic voltage amplifier with a differential input and usually, a single-ended output.



→ It is frequently used to amplify signals in sensor circuit.

→ Also called differential amplifier / Opamps

Inverting Amplifiers

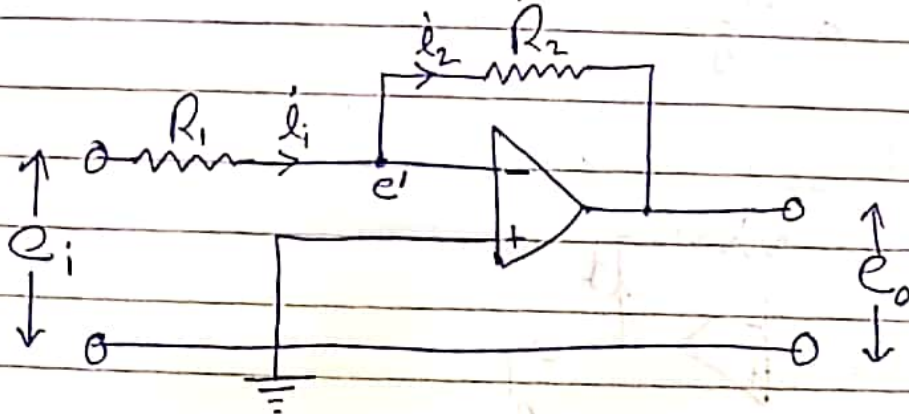

$$i_1 = \frac{e_i - e'}{R_1} \quad i_2 = \frac{e' - e_o}{R_2}$$

Since negligible current flows into the amplifier, the current $i_1 = i_2$

$$\frac{e_i - e'}{R_1} = \frac{e' - e_o}{R_2}$$


$$K(0 - e') = e_o \quad \text{as } K \gg 1 \Rightarrow e' \approx 0$$

$$\text{So } \frac{e_i}{R_1} = -\frac{e_o}{R_2}$$

$$e_o = -\frac{R_2}{R_1} e_i$$

If $R_1 = R_2$, then the opamp circuit shown acts as a sign inverter.

Non inverting Amplifier

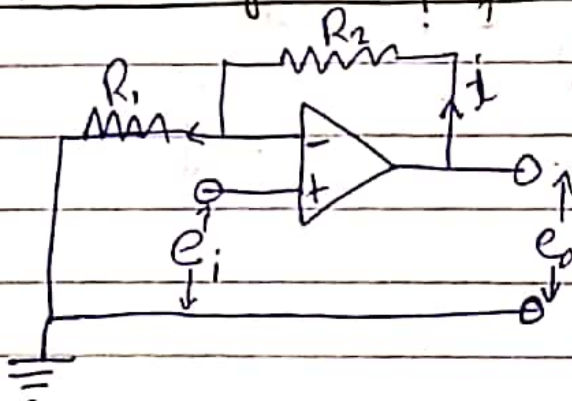

$$e_o = i(R_1 + R_2)$$

$$e_o = K(e_i - iR_1)$$

$$e_o = K\left(e_i - \frac{e_o R_1}{R_1 + R_2}\right)$$


$$e_o\left(1 + \frac{K R_1}{R_1 + R_2}\right) = K e_i$$

$$\frac{e_o}{e_i} = \frac{K}{1 + \frac{K R_1}{R_1 + R_2}}$$

$$\Rightarrow \frac{e_i}{e_o} = \frac{1}{K} + \frac{R_1}{R_1 + R_2} \left\{ \frac{1}{K} \ll \frac{R_1}{R_1 + R_2} \right\}$$

$$\boxed{\frac{e_o}{e_i} = 1 + \frac{R_2}{R_1}}$$

Example 3.8:

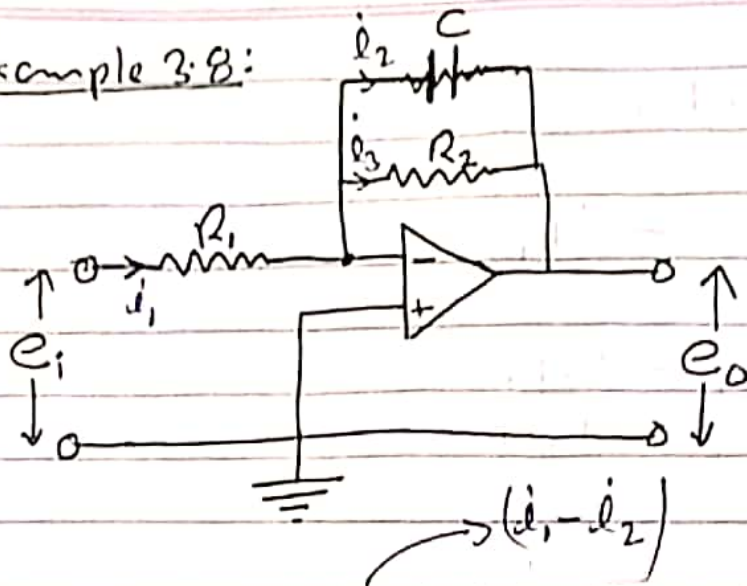

$$-e_i + i_1 R_1 + i_3 R_2 + e_o = 0 \quad \text{--- ①}$$

$$-e_i + i_1 R_1 + \frac{1}{C} \int_0^t i_2 dt = 0 \quad \text{--- ②}$$

$$\left\{ \begin{array}{l} -e_i + i_1 R_1 + e' = 0 \quad \text{--- ③} \\ K(0 - e') = e_o \quad \text{--- ④} \end{array} \right.$$

$$i_1 = i_2 + i_3$$

$$e_o = -K(e_i - i_1 R_1)$$

$$E_o(s) = -K(E_i(s) - I_1(s) R_1)$$

$$-E_i(s) + I_1(s) R_1 + (I_1(s) - I_2(s)) R_2 + E_o(s) = 0$$

$$-E_i(s) + I_1(s) R_1 + \frac{I_2(s)}{CS} = 0$$

$$I_2(s) = (R_1 I_1(s) + E_i(s)) CS$$

$$-E_i(s) + I_i(s)R_1 + I_i(s)R_3 + R_1CS I_i(s)R_3$$

$$-CS R_3 E_i(s) + E_o(s) = 0$$

$$I_i(s) \{ R_1 + R_3 + R_1 R_3 CS \} - E_i(s) \{ 1 + CS R_3 \} + E_o(s) = 0$$

$$E_o(s) = -K E_i(s) + K R_1 \left\{ \frac{E_i(s) \{ 1 + CS R_3 \} - E_o(s)}{R_1 + R_3 + R_1 R_3 CS} \right\}$$

$$\left(E_o(s) + \frac{K R_1}{R_1 + R_3 + R_1 R_3 CS} E_o(s) \right)$$

$$= -K E_i(s) + \frac{K R_1 (1 + CS R_3)}{R_1 + R_3 + R_1 R_3 CS} E_i(s)$$

$$E_o(s) \left\{ R_1 + R_3 + R_1 R_3 CS + K R_1 \right\}$$

$$= K E_i(s) \left\{ \frac{-R_1 R_3 - R_1 R_3 CS + R_1}{R_1 + R_3 + R_1 R_3 CS} \right\}$$


$$\frac{E_o(s)}{E_i(s)} = K \frac{\cancel{K R_1 R_3} \cancel{R_1} - (R_1 + R_3) + (K-1) R_1 R_3 CS}{K R_1 + (R_1 + R_3) + R_1 R_3 CS}$$

$$\frac{E_o(s)}{E_i(s)} = \frac{-KR_3}{K_1R_1 + (R_1 + R_3) + R_1R_3Cs}$$

$$\Rightarrow \frac{-R_3}{R_1 + \frac{R_1 + R_3}{K} + \frac{R_1R_3Cs}{K}}$$

$$\boxed{\frac{E_o(s)}{E_i(s)} = \frac{-R_3}{R_1} \left(\frac{1}{R_3Cs + 1} \right)}$$

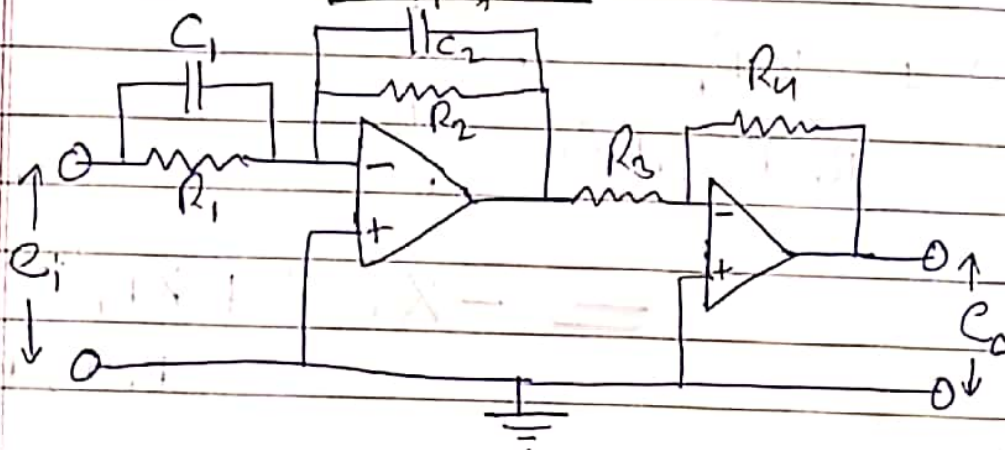
Lead and Lag Network using Operational Amplifiers



$$\boxed{\frac{E_o(s)}{E_i(s)} = \frac{R_4C_1}{R_3C_2} \frac{s + \frac{1}{R_1C_1}}{s + \frac{1}{R_2C_2}}}$$

If $R_1C_1 > R_2C_2 \Rightarrow$ Lead network.
 $R_2C_2 > R_1C_1 \Rightarrow$ Lag network.

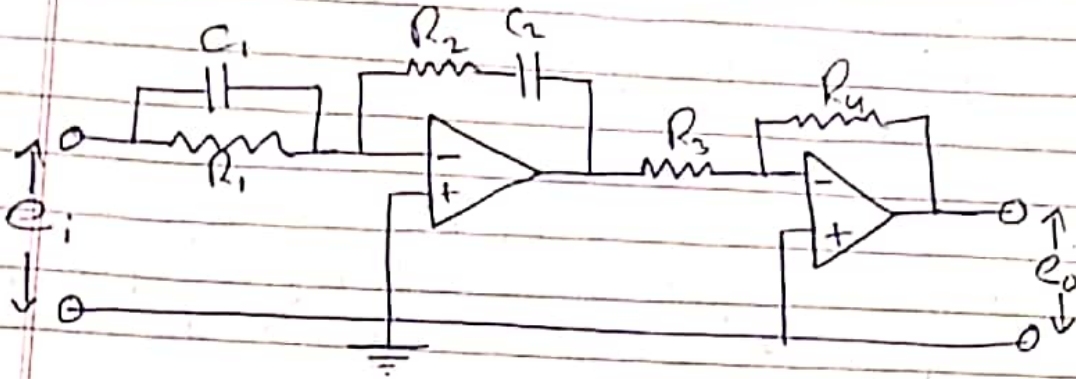PID Controller Using Operational Amplifier



$$\frac{E_o(s)}{E_i(s)} = \frac{R_4(R_1C_1 + R_2C_2)}{R_3R_1C_1} \left[1 + \frac{1}{(R_1C_1 + R_2C_2)s} + \frac{R_1C_1R_2C_2}{R_1C_1 + R_2C_2} s^2 \right]$$

When a PID Controller is expressed as:

$$\frac{E_o(s)}{E_i(s)} = K_p + \frac{K_i}{s} + K_d s$$

$$K_p = \frac{R_4(R_1C_1 + R_2C_2)}{R_3R_1C_1}$$

$$K_i = \frac{R_4}{R_3R_1C_1}$$

$$K_d = \frac{R_4R_2C_1}{R_3}$$